
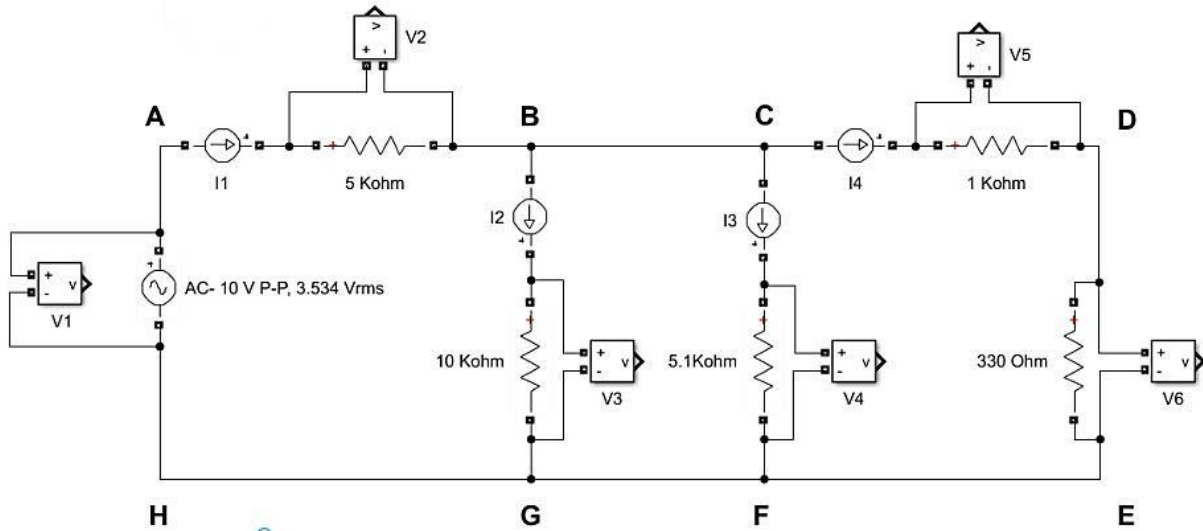


Prove KVL & KCL Laws

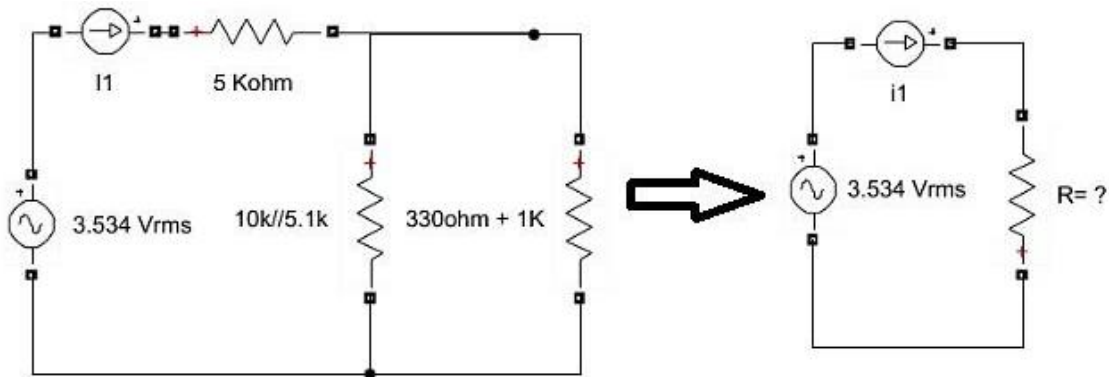

1. Measure Voltage drops across all resistors & find i_1, i_2, i_3, i_4 , currents & prove KVL+ KCL laws.



2. Initially calculate 'i1' current through Equivalent Circuit.


3. For KVL Law, $V_1 = V_2 + V_3$, $V_1 = V_2 + V_4$, $V_1 = V_1 + V_5 + V_6$

4. For KCL Law, $i_1 = i_2 + i_3 + i_4$


Where, i_1 can be found from equivalent circuit or voltage drop across V_2/R or through practical digital multi- meter of NIELVIS-mx Instrument Launcher. Similarly, find other i_2, i_3, i_4 currents from its voltage drop dividing by its resistor.

Prove KVL & KCL Laws

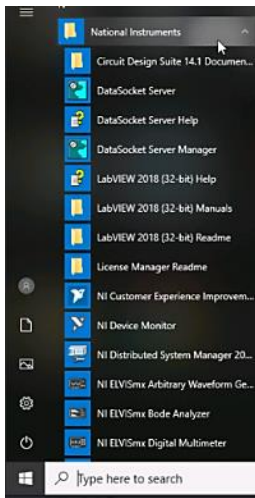
1. Open Electromet and open “NI ELVISmx” as shown in figure.




1. National Instrument

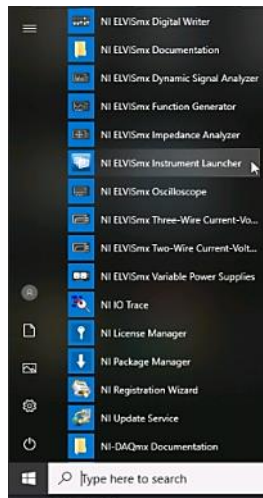


2. NI ELVISmx Instrument

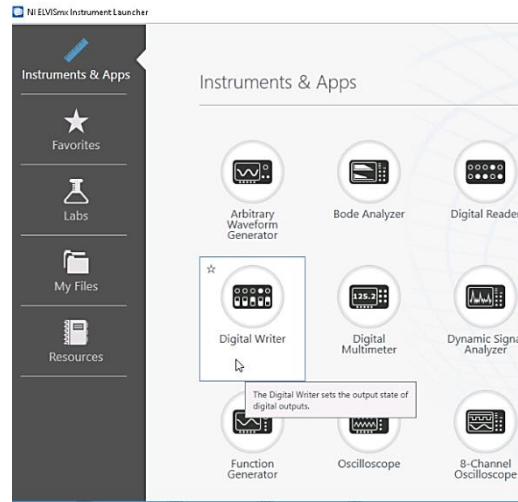


3. NI ELVISmx Instrument Launcher

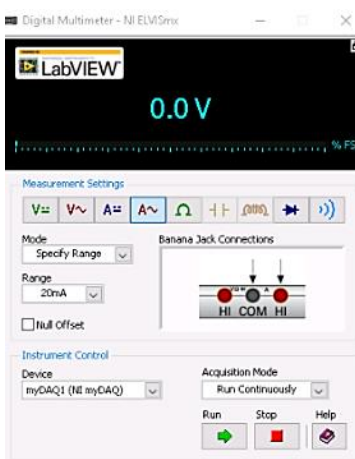

4. Digital Multi-meter for Current I1

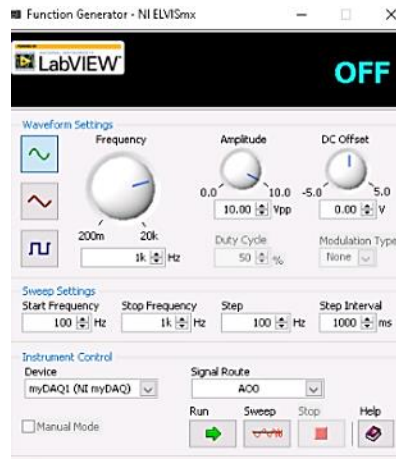


5. Function Generator

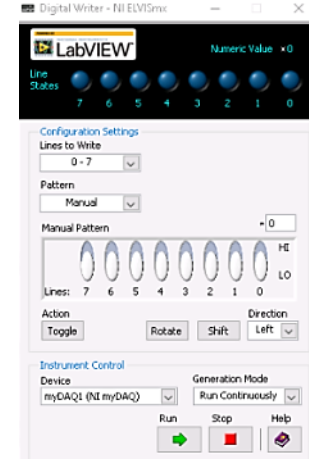

6. Digital Writer (v1 to v6)

Now you should be able to play with all these real NI ELVISmx electronics applications and if there is confusion then ask with the concerned tutor. This is real practical so whatever you change the values it will directly affect the Oscilloscope signals so think before changing and try to find the voltage drop across each resistor and take the pictures of it to verify that you did it well.

Prove KVL & KCL Laws

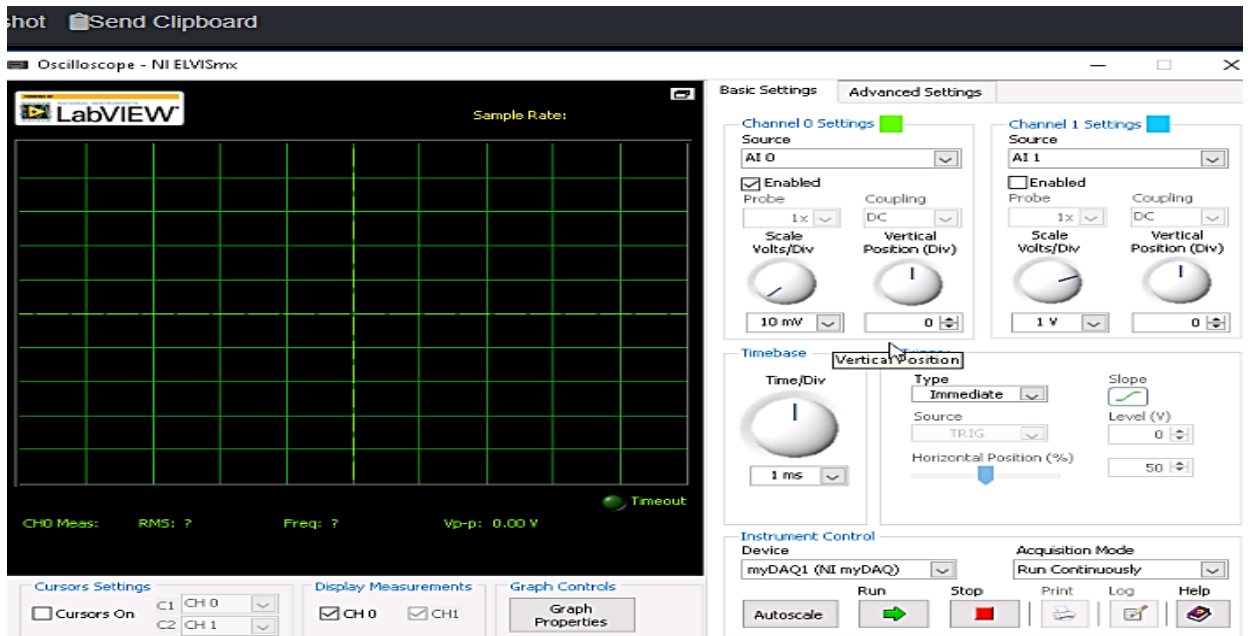



7. Oscilloscope Signal where you can see the RMS Voltages of v1, v2, v3, v4, v5, v6.

Final Steps:

1. Go NI-ELVISmx and open all the functions like Digital Writer, Digital Multi-Meter, Function Generator and Oscilloscope.
2. Open the Function Generator and create frequency 1 KHz with 10 voltage p-p Sinusoidal Signal as shown in above figure.
3. Open the Digital Writer and to see the initial voltage drop signal on 'V1' put the value 0,0,0,1 where you can see the signal in Oscilloscope. Before 0,0,0,1 digital value you cannot see any voltage drop signal in oscilloscope. Similarly find the voltage drop in V2, V3, V4, V5 and V6.
4. Similarly, you can observe 'I1' current from digital meter which should be equal to sum of I2, I3, and I4 if you calculate properly.
5. At last vary the frequency from 1 KHz to 5 KHz or 10 KHz, similarly vary the input ac voltage and find the different currents and voltages to verify KVL & KCL Laws.

Dig 3	Dig2	Dig1	Dig0	Output Voltage
0	0	0	1	V1
0	0	1	1	V2
0	1	0	1	V3
0	1	1	1	V4
1	0	0	1	V5
1	0	1	1	V6

Prove KVL & KCL Laws

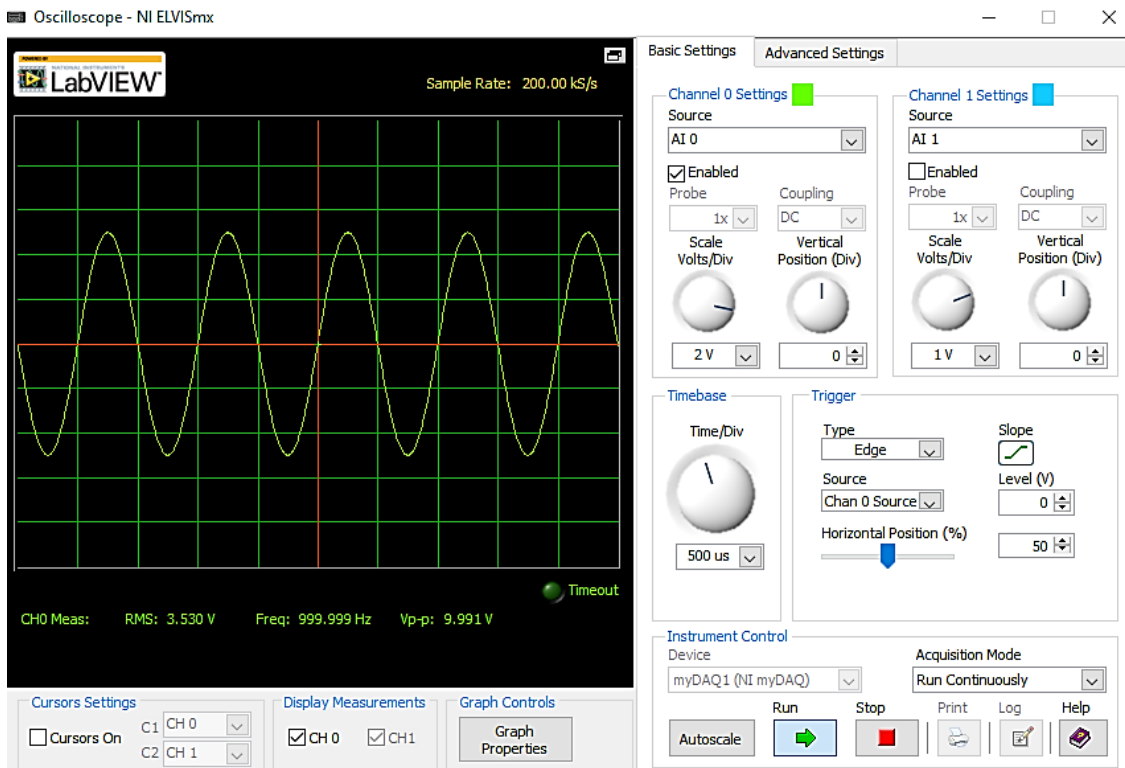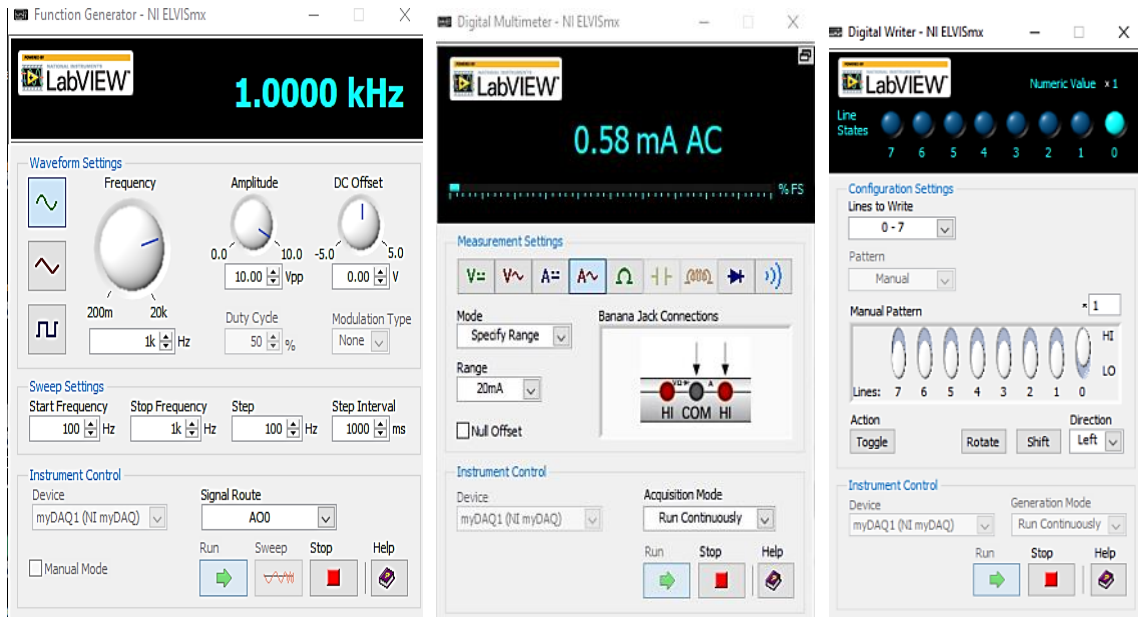

Here, we have done for you one sample that means $i_1 = 0.58 \text{ mA}$ and voltage drop signal $V_{1\text{rms}} = 3.53\text{v}$ and rest i_2, i_3, i_4 and V_2, V_3, V_4, V_5 and V_6 you have to find where you should prove $i_1 = i_2 + i_3 + i_4$ & $V_1 = V_2 + V_3$, $V_1 = V_2 + V_4$ and $V_1 = V_2 + V_5 + V_6$. This will ultimately satisfy KVL and KCL laws.

Thanks