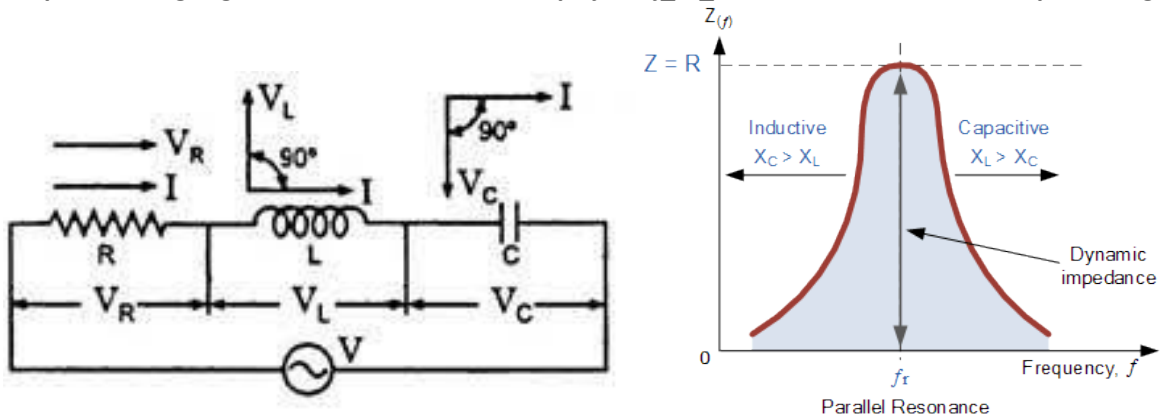


RLC Series Resonance Circuit

https://drive.google.com/file/d/1LGRmAUAgZ5jmE9j_m_R5Ofdw2zDbealC/view?usp=sharing



Given:

L=100mH

C= Try 0.33uf or 0.1uf

R= 120 Ohm

V (pk-pk) = 0.5v

Conditions:

1. The flow of current in inductor and capacitor during resonance frequency should be maximums in compare to other frequencies.
2. The voltage drop on the inductor and capacitor during resonance frequency should be almost equal during frequency resonance
3. The phase of inductor voltage should always lead the voltage of capacitor.
4. During Resonance Frequency the reactance of inductor and capacitor will be equal

$$X_L = X_C \text{ (we will prove it later)}$$

$$X_L = 2\pi fL = 552 \text{ ohm}$$

$$X_C = 1/2\pi fc = 552 \text{ ohm}$$

Formulae:

$$V_L = V_C$$


$$I * X_L = I * X_C \text{ (same series current)}$$

$$\omega L = 1/\omega C$$

$$2\pi * f * L = 1/2\pi * f * C$$

$$f_r = 1/2\pi\sqrt{LC} \text{ (Put the value of Inductor and Capacitor)}$$

f_r = ? (Find Resonance Frequency)

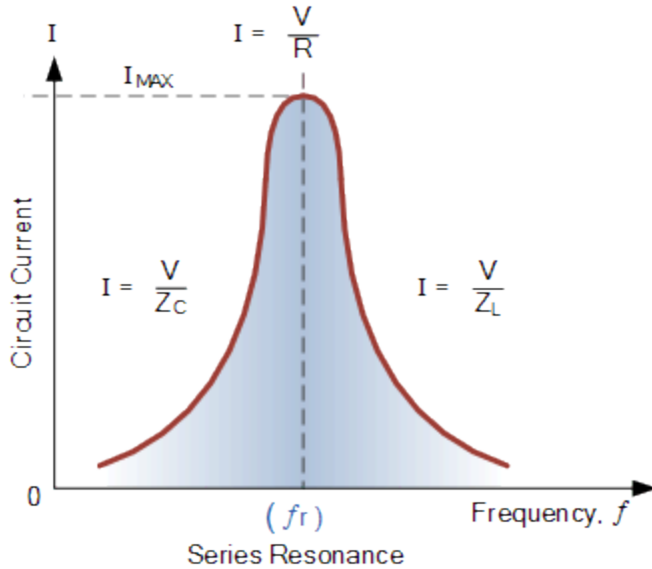

4. The graph should look like this where you can find the resonant current value mathematically through voltage drop across inductor or capacitor during resonance divided by inductor or capacitor reactance.
5. Also bandwidth and quality factor can be calculated through the -3db calculation as well quality factor through series resistor. Please go through theory RLC material if needed more information.
6. Watch short video to learn how to operate RLC series resonance in Electromet.

Thanks